

Lab 8: VGA Display

Due: 18:30, November 29, 2016

Action Item

Modify the Verilog code introduced in class to design a circuit for controlling the VGA display. The controller has the following input ports:

- input clk;
- input reset;
- input en;
- input dir;

Action Item

and the following output ports:

- output [3:0]vgaRed;
- output [3:0]vgaGreen;
- output [3:0]vgaBlue;
- output hsync;
- output vsync;

Action Item

The behavior of the circuit is explained below.

- At the beginning or when pressing the **reset** button, the VGA display will show the image (e.g., kanahei.jpg) at the origin position. It will stay still until the **en** button is pressed.

Action Item

- The image will start/resume scrolling left or right in a column- by-column manner under the frequency of $\text{clk} / 2^{22}$ (i.e., $\text{clk} / 2^{22}$), or pause, depending on whether the number of the **en** button pressed is odd or even. The scrolling direction of the image is determined by **dir** input. If **dir** is 0, the image will scroll left. If **dir** is 1, the image will scroll right.

Example

at the begining
or pressing **reset**



Example

set **SW0** = 1, press **en**
➔ start to scroll right



(100 columns scrolled right)

Example



(200 columns scrolled right)

Example



(400 columns scrolled right)

Example

press **en**
➔ pause



(still 400 columns scrolled right)

Example

set **SW0** = 0, press **en**
➔ resume to scroll left



(400 columns scrolled right and 100 columns scrolled left)